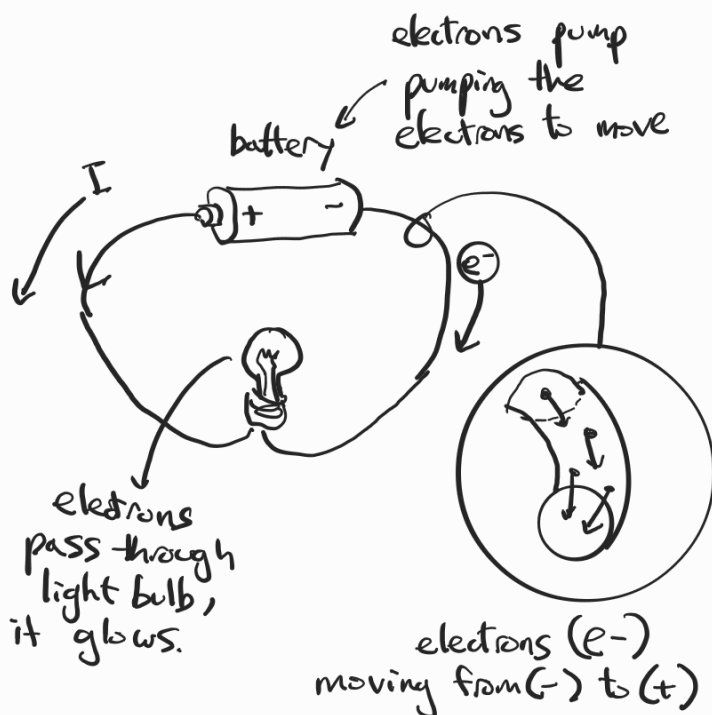


4.2 Circuit and Power

Charge and Current

Set up of a simple circuit:

Note: movement of I current direction is opposite of electrons (-e) flow.



Circuit Symbols

cell 電池

battery

resistor 電阻

variable resistor 可變電阻

light bulb 燈

switch } 開關
push switch }

joint wires

unjoint wires


earth 接地

motor


voltmeter 電壓表

ammeter 電流表

OPEN CIRCUIT
no current

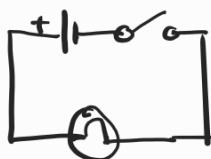

CLOSED CIRCUIT
I current flows

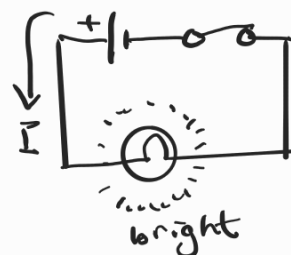

$$I = \frac{Q}{t}$$

↑
current 電流

$$\text{unit: } \frac{C}{s} \Rightarrow A$$

↑
ampere 安培




e.g. $I = 23 A$
(current is 23 ampere)

flow rate 23C of
electrons per second.

flow of current: (+) $\longrightarrow$ (-)
flow of electrons (e-): (-) $\longrightarrow$ (+)


} opposite

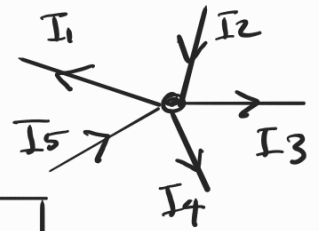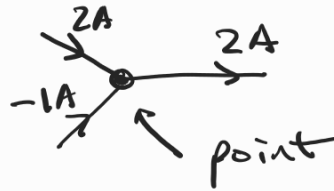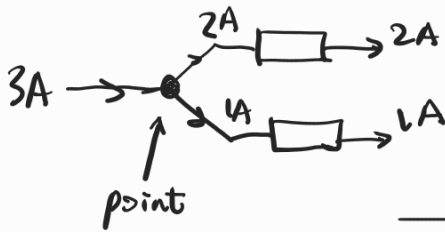At any connection point total current in = total current out




Measuring Current

cut wire, Ammeter in between
電流表

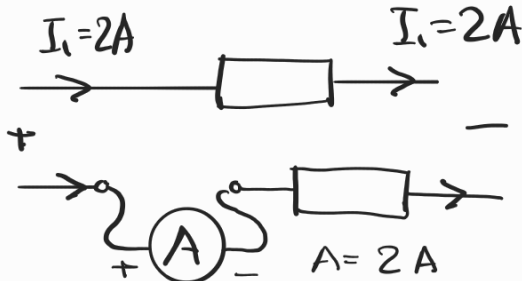
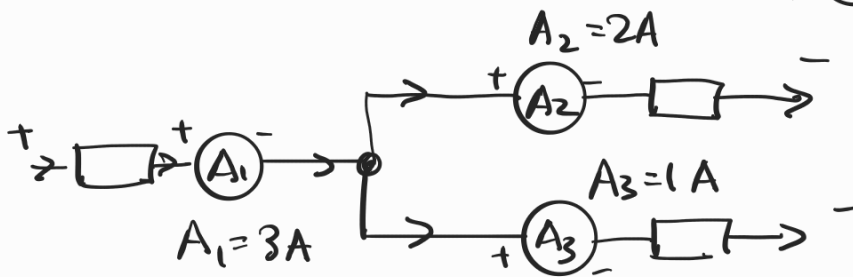
$$\frac{I}{5} + \frac{I}{2} = \frac{I}{1} + \frac{I}{4} + \frac{I}{3}$$




$$A_1 = A_2 + A_3 \quad * \text{ Never overload the ammeter.}$$

Voltage and Energy Transfer

A typical circuit has

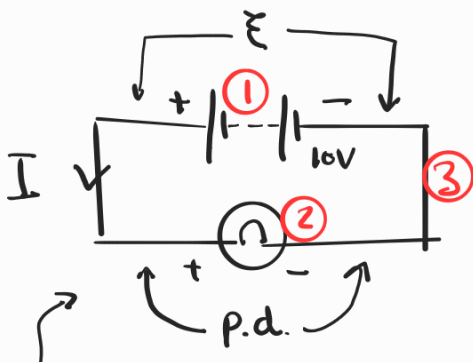- ① Power Sources 電源
- ② loads 負載
- ③ Connecting Wires 電線



$\mathcal{E}$ (電動勢) : Electro Motive Force (by battery)
p.d. : Potential difference (across load)
(電勢差)

In this circuit : $\mathcal{E} = 10V$, p.d. = 10V (both units V, 伏特, volt)

supply side

$$\mathcal{E} = \frac{W}{Q} \quad \begin{array}{l} \text{energy supplied by battery} \\ \text{charge through the battery} \end{array}$$

$\uparrow$
emf


load side

$$V = \frac{W}{Q} \quad \begin{array}{l} \text{energy dissipated by load} \\ \text{charge through load} \end{array}$$


$\uparrow$
p.d

Voltage and Energy Conservation

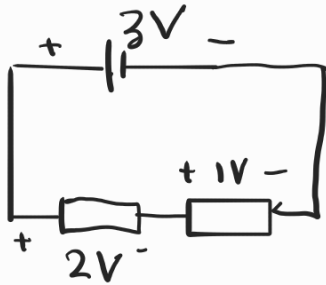For any closed loop, total emf = total p.d.




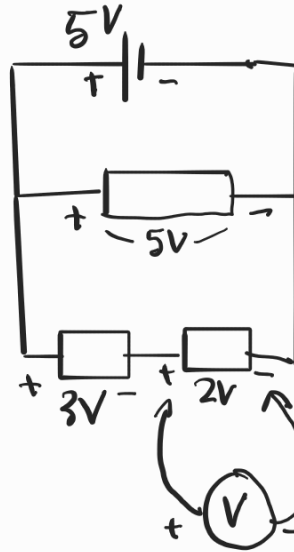measure voltage, use a voltmeter across (+) and (-) terminals



No need to cut wire!

Resistance 电阻

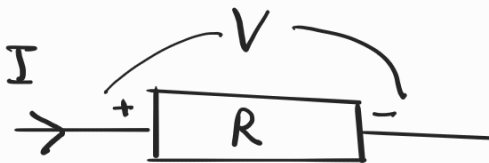


$$V = IR$$

↑ ↑ ↑
电压 电流 电阻
unit: V unit: A
volt ampere

欧姆定律
ohm's law

电阻
unit: Ω ohm

What is a Multi meter? 萬用電表

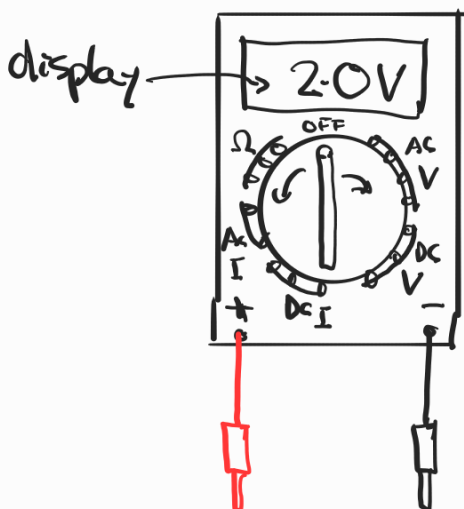


Can measure

resistance : Ω

current : AC and DC

voltage : AC and DC

Resistor

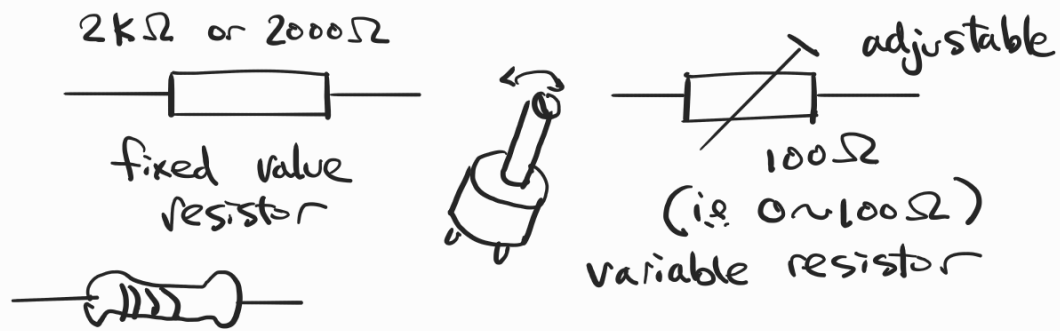


internally, resistor is made up of ohmic material
 歐姆材料

$$R = \rho \frac{L}{A}$$


$$\rho = R \frac{A}{L}$$

(unit of ρ : Ωm)

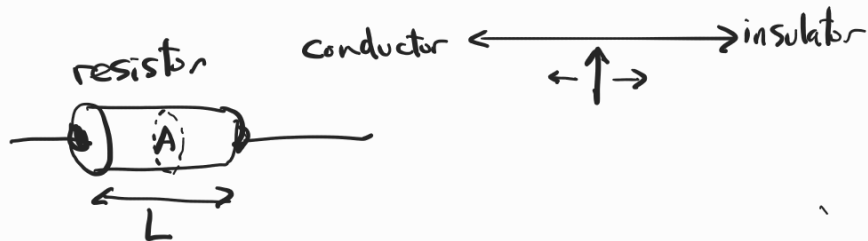


ρ : resistivity 電阻率
 $\frac{1}{\rho}$: conductivity 導電率




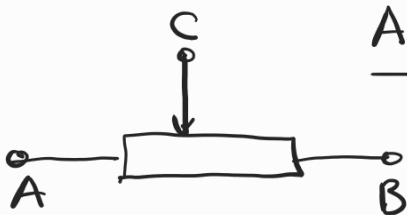
examples of ρ :
gold $2.3 \times 10^{-8} \Omega\text{m}$, graphite $3.5 \times 10^{-5} \Omega\text{m}$ conductors
rubber $10^{13} \Omega\text{m}$, glass $10^{14} \Omega\text{m}$, silicon $10^3 \Omega\text{m}$
insulators ↑ semi-conductor



A variable resistor

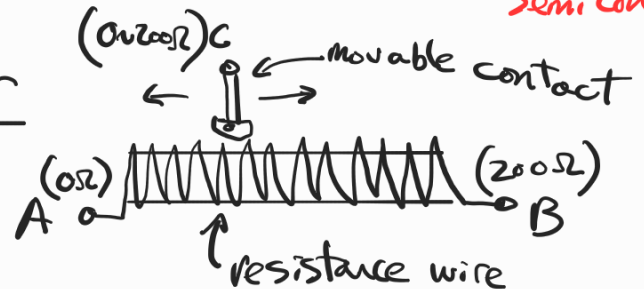


200Ω VR

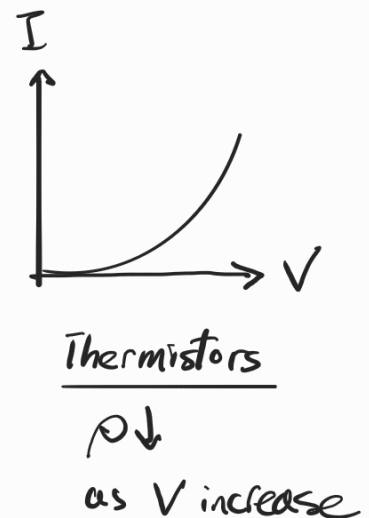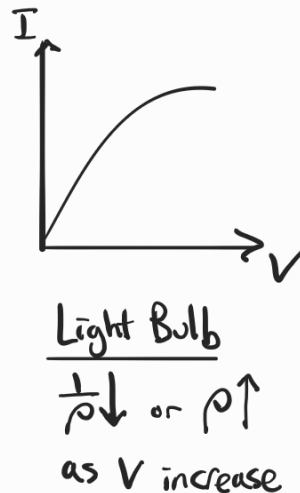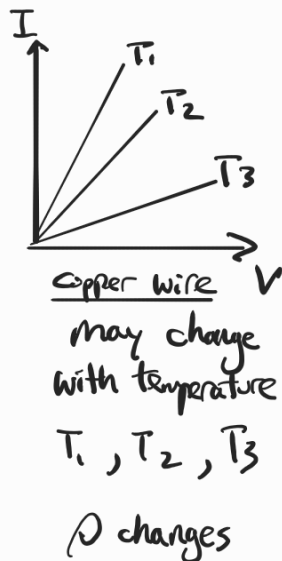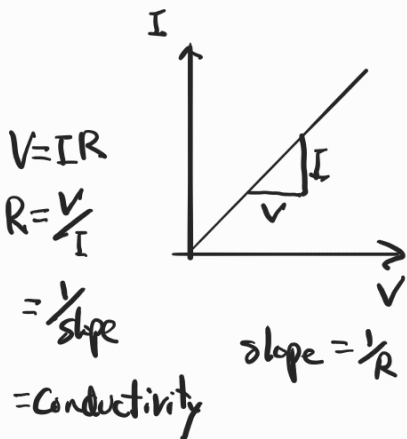


Resistor Networks

$$R = \frac{V}{I}$$

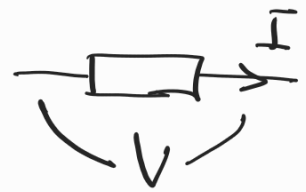


Series connection

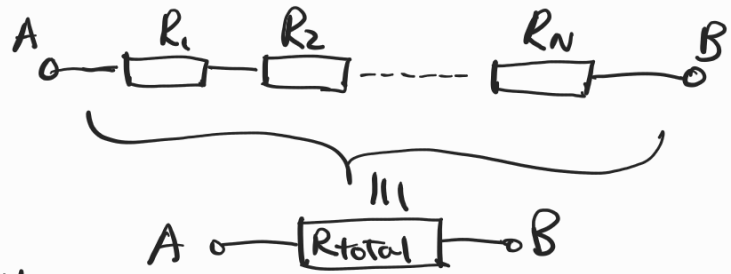

$$R_{\text{total}} = R_1 + R_2 + \dots + R_N$$

Parallel connection

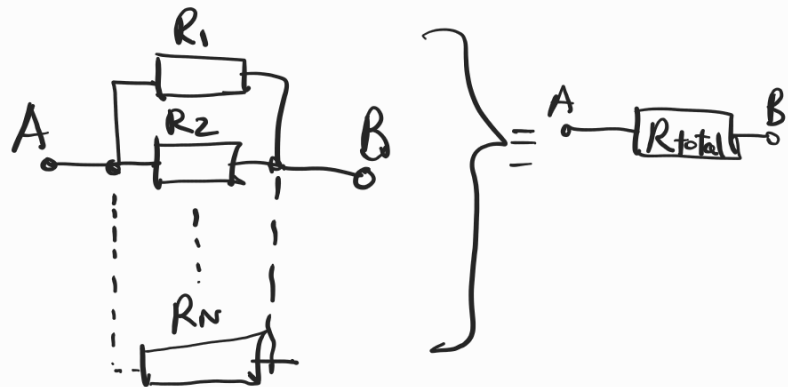


$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$


For 2 resistors parallel connection

$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2}$$
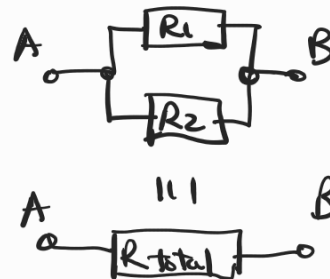
$$\therefore R_{\text{total}} = \frac{R_1 \times R_2}{R_1 + R_2}$$



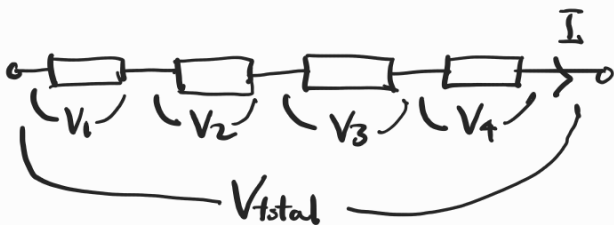
For Series Connection Voltages are shared out to resistors



I : no change

$$V: V_{\text{total}} = V_1 + V_2 + V_3 + V_4$$

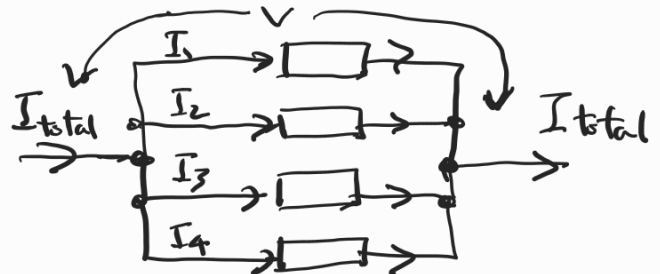
For Parallel Connection Currents are shared out to resistors







$$I: I_{\text{total}} = I_1 + I_2 + I_3 + I_4$$

V : no change

Find the equivalent resistance

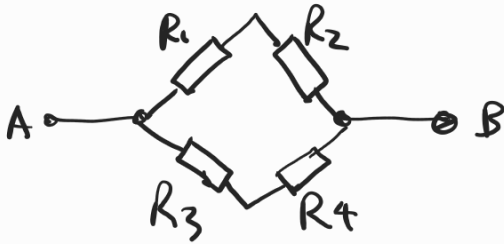
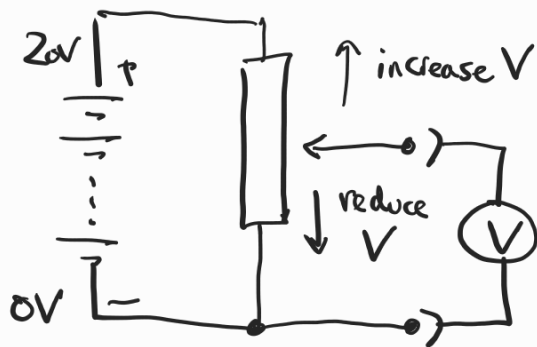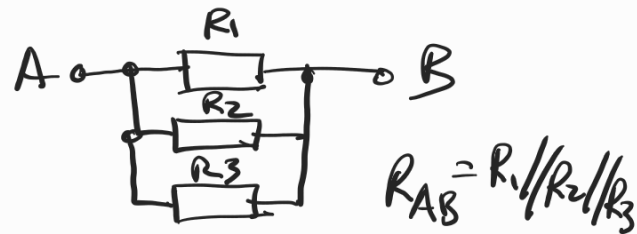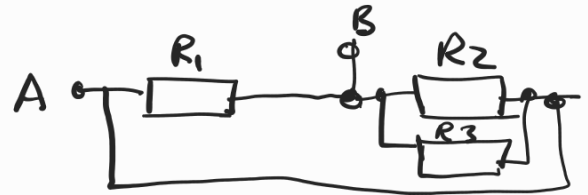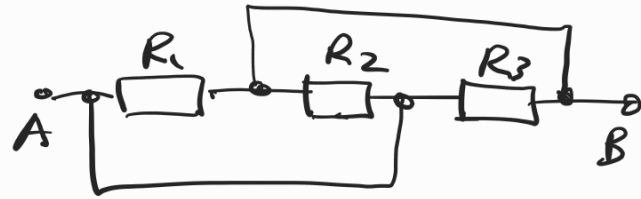
$$R_{AB} = \underbrace{R_1 + R_2}_{\text{in parallel with}} \underbrace{R_3 + R_4}$$



potential divider circuit

Electrical Power

$$\text{Power} = \frac{\text{energy transformed}}{\text{time taken}} \Rightarrow P = \frac{E}{t} \quad \left(\text{unit } \frac{\text{J}}{\text{s}} \right)$$

(unit: W)
watt

$$1 \text{ W} = 1 \text{ J s}^{-1}$$

$$P = V \times I$$

$$P = I^2 R \quad (V = IR \text{ ohm's law})$$

$$P = \frac{V^2}{R} \quad (I = \frac{V}{R} \text{ ohm's law})$$

By conservation of energy : $P_{\text{out}} = P_{\text{in}}$




Practical Cells and Meters

Ideal




Practical

Observation

Battery

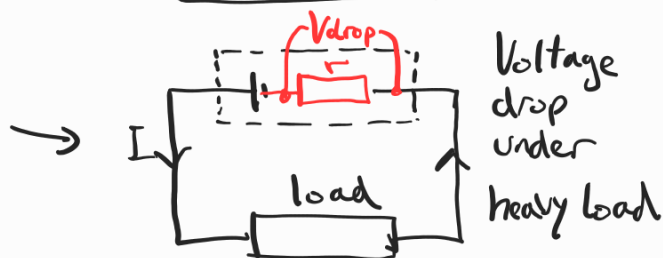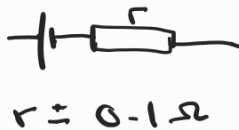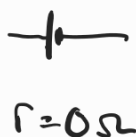

Ammeter

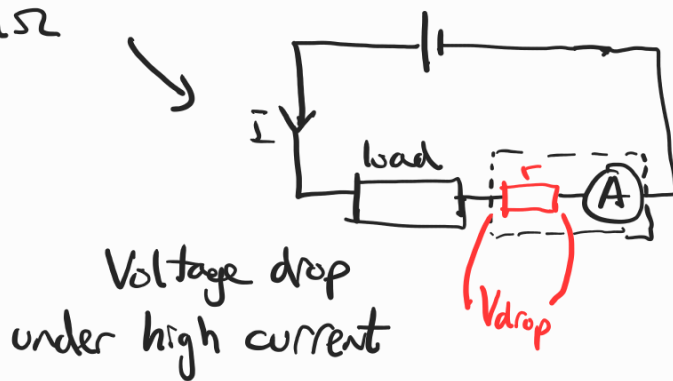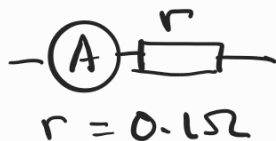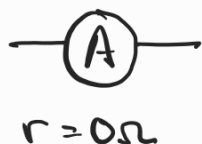

Voltmeter

